

TSEK38: Radio Frequency Transceiver Design

Lecture 5: Low-IF

Ted Johansson, ISY
ted.johansson@liu.se

Lecture schedule

- w4:
- Le1: Introduction (Ch 1)
 - Le2: Fundamentals of RF system modeling (Ch 2)
 - Le3: Superheterodyne TRX design (Ch 3.1)
- w6:
- Le4: Homodyne TRX design (Ch 3.2)
 - **Le5: Low-IF TRX design (Ch 3.3)**
 - Le6: Systematic synthesis (calculations) of RX (Ch 4)
- w7:
- Le7: Systematic synthesis (continued)
 - Le8: Systematic synthesis (calculations) of TX (Ch 5)
- w8:
- Le9: Systematic synthesis (continued)

Lab schedule

- w6:
- We: Lab1a (after Le6): 15-19 (ASGA)
 - Th: Lab1b: 17-21 (SOUT)
- w7:
- We: Lab1c (after Le8): 15-19 (SOUT)
 - Th: Lab1d: 17-21 (EGYP)


- Instructions:
- One long lab (4 x 4 h).
 - Lab manual in the Lisam *Course Documents/2019/Lab* folder.
 - Supervision (Ted) available at the times above.
 - To pass: complete and document the exercises in the lab manual, go through with Ted.

Repetition of Lecture 4

- Direct-Conversion (Zero-IF) Receivers
 - DC offset
 - IP2
 - IQ imbalance (cross-talk)
 - LO leakage
 - 1/f noise

Direct-Conversion (Zero-IF) Receivers

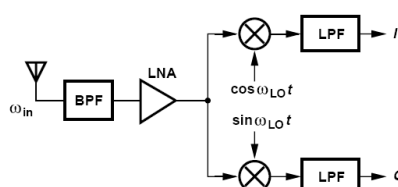- Absence of an image greatly simplifies the design process.
- Channel selection is performed by on-chip low-pass filter.
- Mixing spurs are considerably reduced in number.
- Suitable for ICs, few external components.



Direct-Conversion (Zero-IF) Receivers

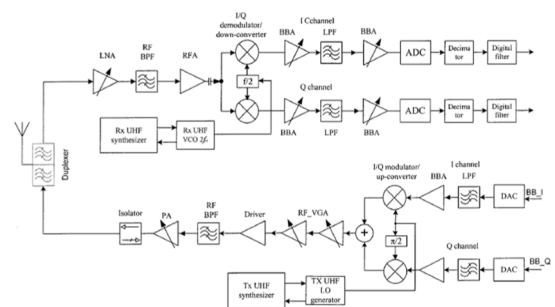


Figure 3.10. Block diagram of direct-conversion transceiver


Frequency plan

RX synthesizer:

- operates at twice f_{RX} to generate IQ and avoid VCO pulling.
- If TX synthesizer is a separate chip the same technique can be used.

TX synthesizer:

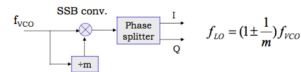
- when integrated it should be designed to avoid VCO reverse modulation (2nd harmonic of TX can pull VCO at twice f_{TX}).
- Preferred is offset technique.



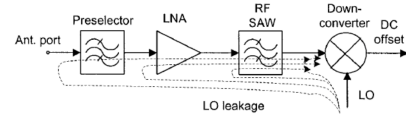3.2.2.1 DC offsets

A finite amount of in-band LO leakage appears at the LNA input. Along with the desired signal, this component is amplified and mixed with LO.


May saturate baseband circuits, simply prohibiting signal detection. Also for the superheterodyne but much more severe with direct-conversion because of high BB gain (70-80 dB), so even a small offset (250 μ V DC at the downconverter) can overload the ADC.



LO self-mixing


DC offsets

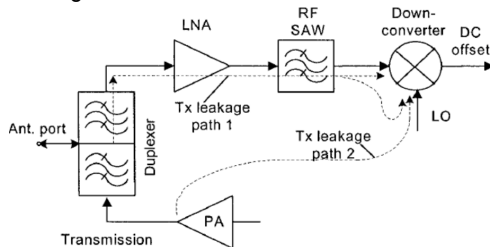Another possible mixing problem: transmission leakage self-mixing.



DC offsets

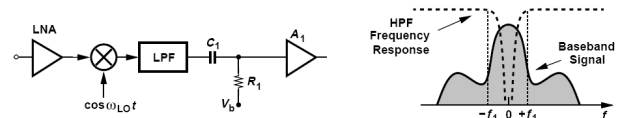- Cancellation: AC coupling, high-pass filters.
- Will also remove a fraction of the signal's spectrum near zero frequency, introducing ISI (3.2.3.1).



- But corner frequency has to be very low ($f_{BB}/1000$) $\Rightarrow$, C_1 may be very large and not suitable for integration.
- Many other solutions (circuit, architectures, calibration) also exist for this problem.

DC offset cancellation (time variant)


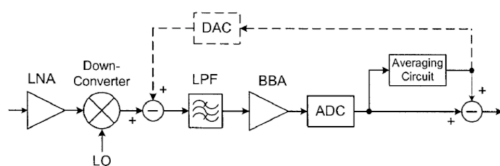


Figure 3.14. A possible configuration of DC offset cancellation


- Active DC offset cancellation by digital feedback, 4-6 bit DACs.
- Also $1/f$ noise partly reduced.

IP2 considerations (partially 3.2.3.2)

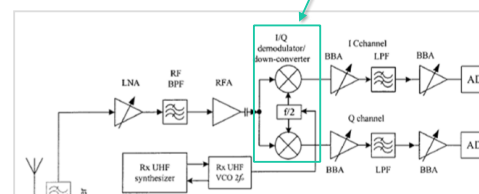
- High IIP2 is needed in direct-conversion receivers.
 - 2nd order distortion by LNA and RFA easy to block with the RF BPF and AC coupling cap.
- $\Rightarrow$ IIP2 RX mostly given by the IQ down-converters.




2nd order distortion

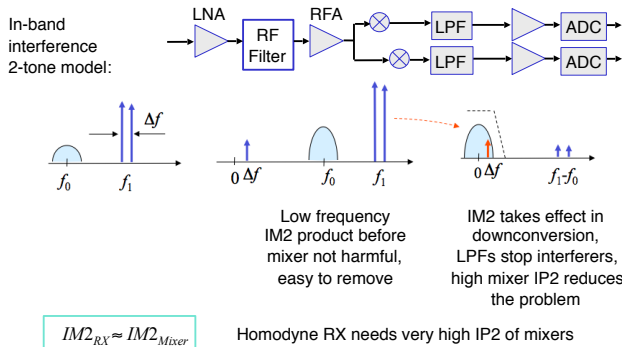

IQ mismatch (imbalance)

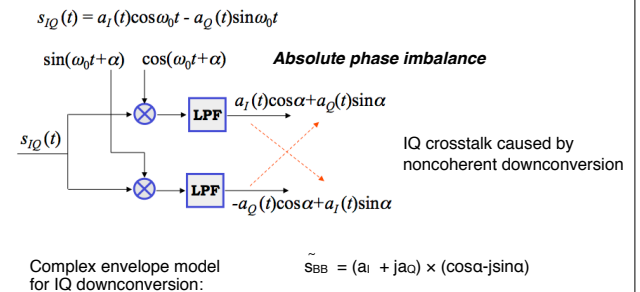


QPSK simulation example: IQ crosstalk

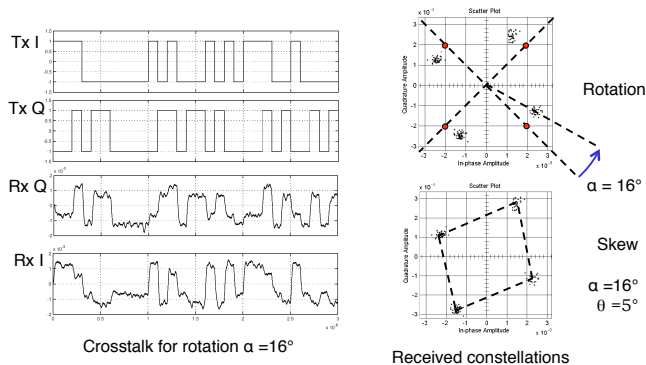


LO leakage emission

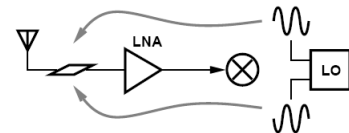- Allowable emission level: -60 to -80 dBm
 - LO input level to mixer: -5 to 0 dBm
 - Reverse isolation to get < -80 dBm $\Rightarrow$ > 85 dB
 - LO leakage can be minimized through symmetric layout of the oscillator and the RF signal path.
- $\Rightarrow$ LO leakage arises primarily from random or deterministic asymmetries in the circuits and the LO waveform.



Flicker noise

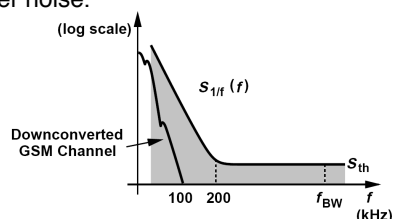- Since the signal is centered around zero frequency, it can be substantially corrupted by flicker noise.




- Fix: lower 1/f noise, NF optimization of RX chain.

Summary

- Homodyne RX well suited for integration.
- Challenged by DC offset, high demands on IP2, 1/f noise.
- No image problem in RX.
- Most of the IP2-requirements are given by the down-conversion mixer,
- Homodyne TX simple – one step – but challenges by possible pulling of LO.

Close-image problem

25

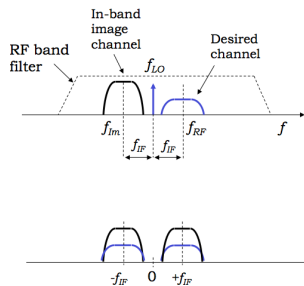


Tough requirements for IQ match if image is large, otherwise signal strongly corrupted

$$f_{IF} = \frac{1}{2} BW \text{ typical}$$

Trade-off in choice of IF

26

- High IF

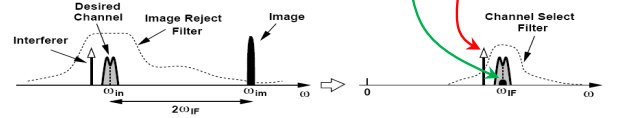

- Low IF


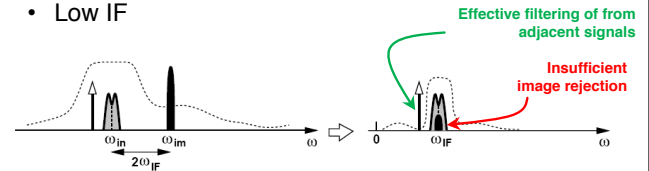


Image Rejection Ratio

27

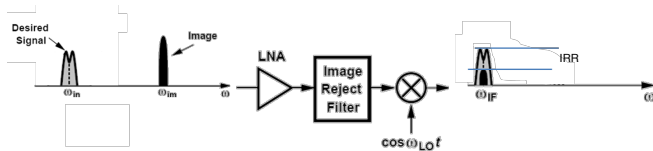- Image Rejection Ratio, IRR = (Power of the received signal)/(Power of the image signal) at the IF port
- Since IRR is a ratio, it is often expressed in dB.




IQ imbalance and Image rejection (3.3.2.1)

28

$$IRR = 10 \log \frac{P_{\text{Signal}}}{P_{\text{Image}}}$$

$$IRR = 10 \log \frac{1 + 2(1 + \delta) \cos \varepsilon + (1 + \delta)^2}{1 - 2(1 + \delta) \cos \varepsilon + (1 + \delta)^2}$$

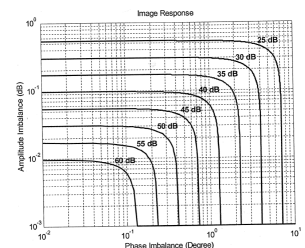δ - amplitude (gain) imbalance
 ε - phase imbalance



IR is partly insensitive, e.g. for 0.3dB gain imbalance, IRR=30dB keeps up to 2° phase imbalance

High IRR

29

- 3.3.2.2 Calibration of IQ (analog) in the RX + Digital Dual Quadrature Down-Converter Approach (baseband) (Fig. 3.21),
- complicated,
- IRR > 50 dB,
- can not be used with Full-Duplex.
- 3.3.2.2(again !) (analog) No calibration + Polyphase Band-Pass Filter Approach (directly after the mixer),
- power hungry,
- IRR > 40 dB.

Summary

30

- Low-IF RX is a tradeoff between heterodyne and homodyne.
- Blocking profile dictates $IF = BW/2$.
- DC offset and $1/f$ noise issues are reduced but close-in image is introduced.
- Image rejection in Low-IF RX more challenging than in homodyne RX.
- IQ correction and IR convenient after ADC.
- Good for narrow-band standards like GSM.

www.liu.se